

Counter in Gray code, variable number of bits, up/down, reset

Gray code 3 bit up counter

| Dec | Present state | | | Next state | | |
|-----|---------------|-------|-------|------------|-------|-------|
| | q_2 | q_1 | q_0 | d_2 | d_1 | d_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 2 | 0 | 1 | 1 | 0 | 1 | 0 |
| 3 | 0 | 1 | 0 | 1 | 1 | 0 |
| 4 | 1 | 1 | 0 | 1 | 1 | 1 |
| 5 | 1 | 1 | 1 | 1 | 0 | 1 |
| 6 | 1 | 0 | 1 | 1 | 0 | 0 |
| 7 | 1 | 0 | 0 | 0 | 0 | 0 |

d_2 :

| | | | | | |
|-------|---|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 0 | 0 | 0 | 1 |
| | 1 | 0 | 1 | 1 | 1 |

$$d_2 = q_2q_0 + q_1/q_0$$

d_1 :

| | | | | | |
|-------|---|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 0 | 1 | 1 | 1 |
| | 1 | 0 | 0 | 0 | 1 |

$$d_1 = /q_2q_0 + q_1/q_0$$

d_0 :

| | | | | | |
|-------|---|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 1 | 0 | 0 |

Gray code 3 bit down counter

| Dec | Present state | | | Next state | | |
|-----|---------------|-------|-------|------------|-------|-------|
| | q_2 | q_1 | q_0 | d_2 | d_1 | d_0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 7 | 1 | 0 | 0 | 1 | 0 | 1 |
| 6 | 1 | 0 | 1 | 1 | 1 | 1 |
| 5 | 1 | 1 | 1 | 1 | 1 | 0 |
| 4 | 1 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0 | 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |

K maps

d_2 :

| | | | | | |
|-------|---|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 |

$$d_2 = /q_1/q_0 + q_2q_0$$

d_1 :

| | | q_1q_0 | | | |
|-------|---|----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 0 | 0 | 0 | 1 |
| | 1 | 0 | 1 | 1 | 1 |

$$d_1 = q_2q_0 + q_1/q_0$$

d_0 :

| | | q_1q_0 | | | |
|-------|---|----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| q_2 | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 1 | 0 | 0 |

$$d_0 = q_2/q_1 + /q_2q_1$$

Gray code 4 bit up counter

| Dec | Present state | | | | Next state | | | |
|-----|---------------|-------|-------|-------|------------|-------|-------|-------|
| | q_3 | q_2 | q_1 | q_0 | d_3 | d_2 | d_1 | d_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 4 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 5 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 7 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 8 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 9 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 11 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 12 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 13 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 14 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 15 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

d_3 :

| | | | | | |
|----------|----|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_3q_2 | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 0 | 0 | 0 |
| | 11 | 1 | 1 | 1 | 1 |
| | 10 | 0 | 1 | 1 | 1 |

$$d_3 = q_2/q_1/q_0 + q_3q_0 + q_3q_1$$

d_2 :

| | | | | |
|-------------|----------|----|----|----|
| | q_1q_0 | | | |
| | 00 | 01 | 11 | 10 |
| q_3q_2 00 | 0 | 0 | 0 | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 0 |
| 10 | 0 | 0 | 0 | 0 |

$$d_2 = q_2/q_1 + q_2q_0 + /q_3q_1/q_0$$

d_1 :

| | | | | |
|-------------|----------|----|----|----|
| | q_1q_0 | | | |
| | 00 | 01 | 11 | 10 |
| q_3q_2 00 | 0 | 1 | 1 | 1 |
| 01 | 0 | 0 | 0 | 1 |
| 11 | 0 | 1 | 1 | 1 |
| 10 | 0 | 0 | 0 | 1 |

$$d_1 = /q_3/q_2q_0 + q_3q_2q_0 + q_1/q_0$$

d_0 :

| | | | | |
|-------------|----------|----|----|----|
| | q_1q_0 | | | |
| | 00 | 01 | 11 | 10 |
| q_3q_2 00 | 1 | 1 | 0 | 0 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 1 | 1 | 0 | 0 |
| 10 | 0 | 0 | 1 | 1 |

$$d_0 = \neg q_3 \neg q_2 q_1 + \neg q_3 q_2 q_1 + q_3 \neg q_2 q_1 + q_3 q_2 q_1$$

Gray code 4 bit down counter

| Dec | Present state | | | | Next state | | | |
|-----|---------------|-------|-------|-------|------------|-------|-------|-------|
| | q_3 | q_2 | q_1 | q_0 | d_3 | d_2 | d_1 | d_0 |
| 15 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 14 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 13 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 0 |
| 12 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| 11 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 9 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 8 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 7 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 5 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 4 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |

d_3 :

| | | | | | |
|----------|----|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_3q_2 | 00 | 1 | 0 | 0 | 0 |
| | 01 | 0 | 0 | 0 | 0 |
| | 11 | 0 | 1 | 1 | 1 |
| | 10 | 1 | 1 | 1 | 1 |

$$d_3 = \neg q_2 / q_1 / q_0 + q_3 / q_1 q_0 + q_3 q$$

d_2 :

| | | | | | |
|----------|----|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_3q_2 | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 1 | 1 | 0 |
| | 11 | 1 | 1 | 1 | 1 |
| | 10 | 0 | 0 | 0 | 1 |

$$d_2 = q_2/q_1 + q_2q_1q_0 + q_3q_1/q_0$$

d_1 :

| | | | | | |
|----------|----|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_3q_2 | 00 | 0 | 0 | 0 | 1 |
| | 01 | 0 | 1 | 1 | 1 |
| | 11 | 0 | 0 | 0 | 1 |
| | 10 | 0 | 1 | 1 | 1 |


$$d_1 = /q_3q_2q_0 + q_3/q_2q_0 + q_1/q_0$$


d_0

| | | | | | |
|----------|----|----------|----|----|----|
| | | q_1q_0 | | | |
| | | 00 | 01 | 11 | 10 |
| q_3q_2 | 00 | 0 | 0 | 1 | 1 |
| | 01 | 1 | 1 | 0 | 0 |
| | 11 | 0 | 0 | 1 | 1 |
| | 10 | 1 | 1 | 0 | 0 |

$$d_0 = \neg q_3/q_2q_1 + \neg q_3q_2/q_1 + q_3q_2q_1 + q_3/q_2/q_1$$

Schematic diagram

 

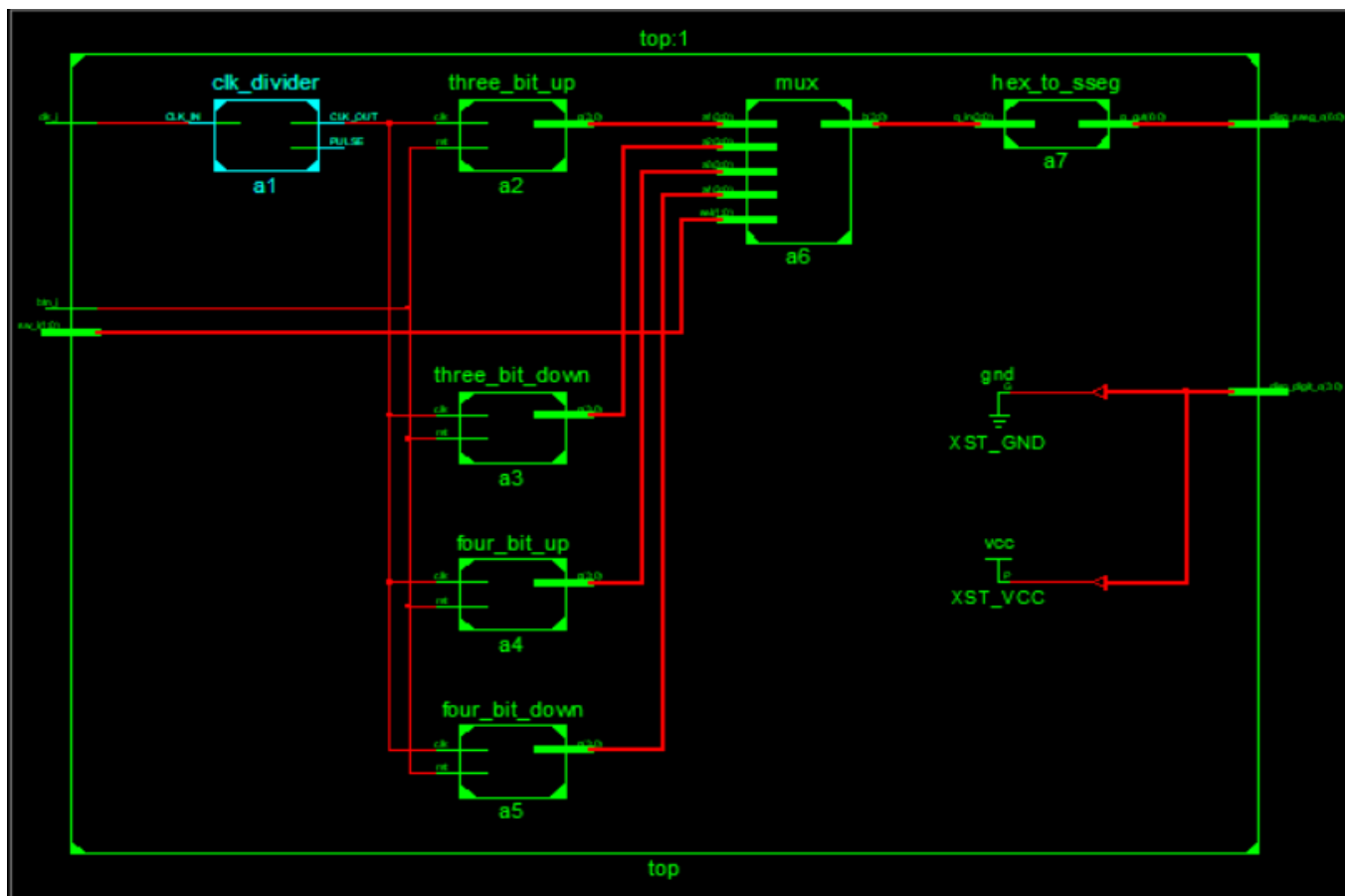

3 bit up counter

```
30      --s
31      process(clk,rst,d)
32      begin
33          if rst = '0' then
34              counter<="0000";
35          elsif (clk'event and clk='1') then
36              if counter = "0100" then
37                  counter<="0000";
38              else
39                  counter<=d;
40              end if;
41          end if;
42      end if;
43      end process;
44
45      --k
46      process(counter)
47      begin
48          d(3)<= '0';
49          d(2) <= (counter(2) and (not counter(1))) or (counter(2) and counter(0)) or ((not
50              counter(3)) and counter(1) and (not counter(0)));
51          d(1) <= ((not counter(3)) and (not counter(2)) and counter(0)) or (counter(3) and
52              counter(2) and counter(0)) or (counter(1) and (not counter(0))) ;
53          d(0) <= ((not counter(3)) and (not counter(2)) and (not counter(1))) or ((not
54              counter(3)) and counter(2) and counter(1)) or (counter(3) and counter(2) and (not
55              counter(1)) or (counter(3) and (not counter(2)) and counter(1)) ;
56      end process;
```

Main file code

```
2      library IEEE;
3      use IEEE.STD_LOGIC_1164.ALL;
4      use ieee.std_logic_unsigned.all;
5
6      entity top is
7      Port(      clk_i: in std_logic;
8              btn_i: in std_logic;
9              sw_i: in std_logic_vector(1 downto 0);
10             disp_sseg_o: out std_logic_vector(6 downto 0);
11             disp_digit_o : out std_logic_vector(4-1 downto 0)
12             );
13      end top;
14
15      architecture Behavioral of top is
16
17          -----
18          component clk_divider is
19              generic (DIVIDER : positive :=8000);
20              Port
21                  (CLK_IN  : in std_logic;
22                   CLK_OUT : out std_logic;
23                   PULSE   : out std_logic
24                  );
25          end component;
26          -----
27          component three_bit_up is
28              Port
29                  (clk: in std_logic;
30                   rst: in std_logic;
31                   q: out std_logic_vector(3 downto 0)
32                  );
33          end component;
34          -----
35          component three_bit_down is
36              Port
37                  (clk: in std_logic;
38                   rst: std_logic;
39                   q: out std_logic_vector(3 downto 0)
40                  );
41          end component;
42          -----
43          component four_bit_up is
44              Port
45                  (clk: in std_logic;
46                   rst: std_logic;
47                   q: out std_logic_vector(3 downto 0)
48                  );
49          end component;
50          -----
51          component four_bit_down is
52              Port
53                  (clk: in std_logic;
```

```

49     port      (clk: in std_logic;
50                rst: std_logic;
51                q  : out std_logic_vector(3 downto 0)
52                );
53 end component;
54 -----
55
56 component hex_to_sseq is
57     port(q_in : in  STD_LOGIC_VECTOR(3 downto 0);

```

```

58         q_out: out STD_LOGIC_VECTOR(6 downto 0)
59         );
60 end component;
61 -----
62     component mux is
63     port(
64         a1      : in  std_logic_vector(3 downto 0);
65         a2      : in  std_logic_vector(3 downto 0);
66         a3      : in  std_logic_vector(3 downto 0);
67         a4      : in  std_logic_vector(3 downto 0);
68         sel     : in  std_logic_vector(1 downto 0);
69         b       : out std_logic_vector(3 downto 0));
70 end component;
71 -----
72     signal clk_1Hz_s : std_logic;
73     signal q_s       : std_logic_vector(3 downto 0);
74     signal q_sd      : std_logic_vector(3 downto 0);
75     signal q_s4bu    : std_logic_vector(3 downto 0);
76     signal q_s4bd    : std_logic_vector(3 downto 0);
77     signal q_dec_out : std_logic_vector(6 downto 0);
78     signal q_mux_out : std_logic_vector(3 downto 0);
79
80 begin
81     a1: clk_divider generic map(DIVIDER=>8000)
82         port map(CLK_IN=>clk_i, CLK_OUT=>clk_1Hz_s);
83     a2: three_bit_up port map(clk=>clk_1Hz_s, rst=>btn_i, q=>q_s);
84     a3: three_bit_down port map(clk=>clk_1Hz_s, rst=>btn_i, q=>q_sd);
85     a4: four_bit_up port map(clk=>clk_1Hz_s, rst=>btn_i, q=>q_s4bu);
86     a5: four_bit_down port map(clk=>clk_1Hz_s, rst=>btn_i, q=>q_s4bd);
87     a6: mux port map(a1=>q_s, a2=>q_sd, a3=>q_s4bu, a4=>q_s4bd, sel=>sw_i, b=>q_mux_out);
88     a7: hex_to_sseq port map(q_in=>q_mux_out, q_out=>q_dec_out);
89     disp_sseq_o<=q_dec_out;
90     disp_digit_o<="1110";
91
92 end Behavioral;

```
